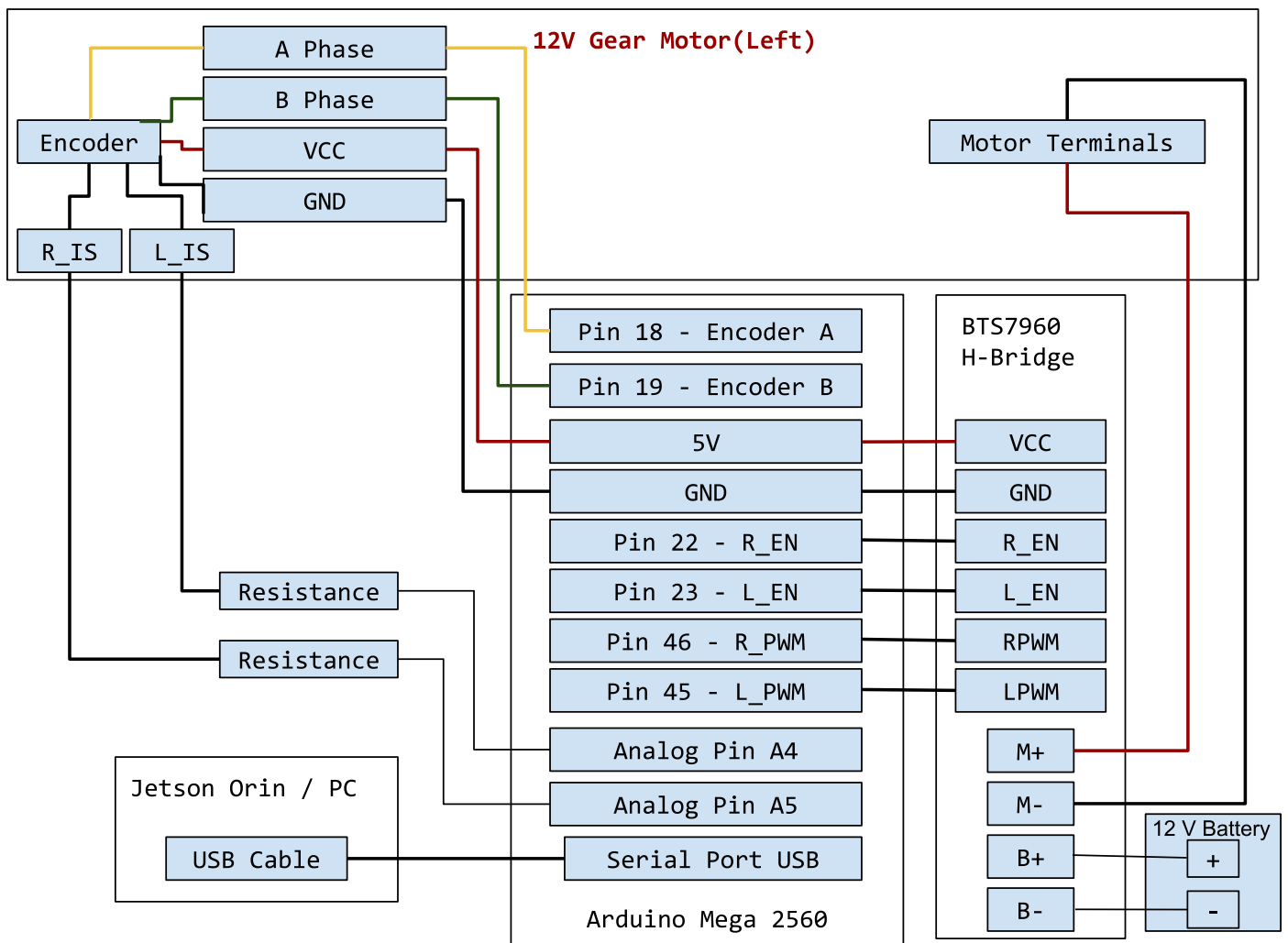


# Hardware Architecture & Wiring(Left Motor)




**Safety Resistors:** You MUST place a 4.7k $\Omega$  - 10k $\Omega$  resistor between the Driver IS pins and the Arduino Analog pins to protect the CPU.

**Interrupts:** Left Motor Encoder A MUST go to Pin 18. Do not swap with Pin 19.

**Common Ground:** Ensure the 12V Battery GND and Arduino GND are connected.
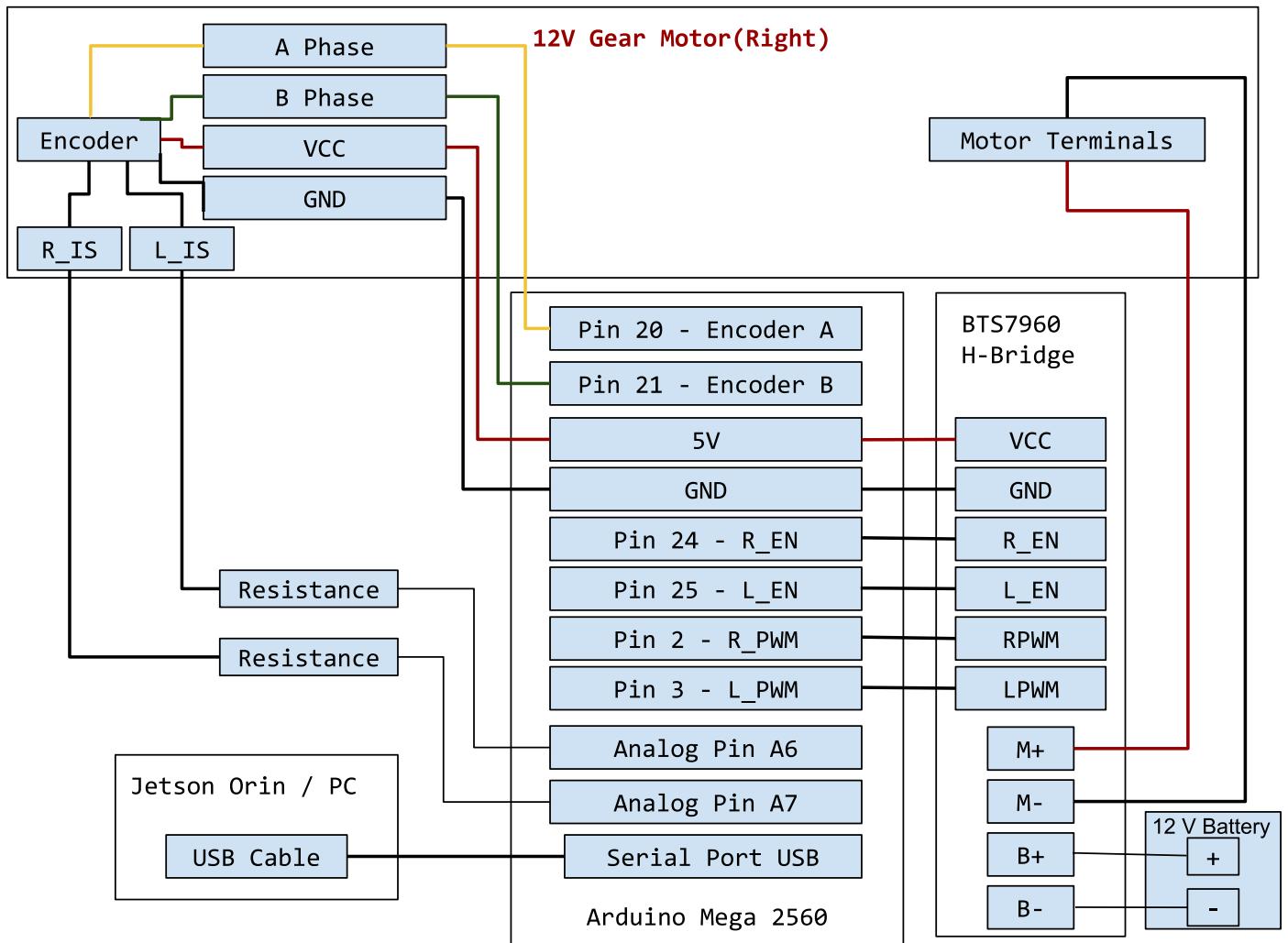
# Hardware Architecture & Wiring(Left Motor)



**Safety Resistors:** You MUST place a  $4.7k\Omega$  -  $10k\Omega$  resistor between the Driver IS pins and the Arduino Analog pins to protect the CPU.

**Interrupts:** Right Motor Encoder A MUST go to Pin 20. Do not swap with Pin 21.

**Common Ground:** Ensure the 12V Battery GND and Arduino GND are connected.